 


## Building Computer Circuits

### Chapter 4.4



---

---

---

---

---

---

---

---

## Purpose

- We have looked at so far how to build logic gates from transistors.
- Next we will look at how to build circuits from logic gates, for example:
  - A circuit to check if two numbers are equal.
  - A circuit to add two numbers.
- Gates will become our new building blocks:
  - Human body: cells → organs → body
  - Computers: gates → circuits → computer

CMPUT101 Introduction to Computing

(c) Yngvi Björnsson

2

---

---

---

---

---

---

---

---

## Circuit

- A circuit is a collection of interconnected logic gates:
  - that transforms a set of binary inputs into a set of binary outputs, and
  - where the values of the outputs depend only on the current values of the inputs
- These kind of circuits are more accurately called combinatorial circuits.

CMPUT101 Introduction to Computing

(c) Yngvi Björnsson

3

---

---

---

---

---

---

---

---

### Circuit (external view)

- A circuit can have any number of inputs and outputs:
  - Number of inputs and outputs can differ.
  - The inputs and outputs are either 0 or 1.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 4

---

---

---

---

---

---

---

---

### Circuit (external view cont.)

- Output depends only on current input values
  - Each set of input always generates the same output.
  - Different sets of input can generate identical output.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 5

---

---

---

---

---

---

---

---

### Circuit (Internal view)

- Circuits are built from interconnected AND, OR and NOT gates, in a way such that each input combination produces the desired output.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 6

---

---

---

---

---


---

---

---

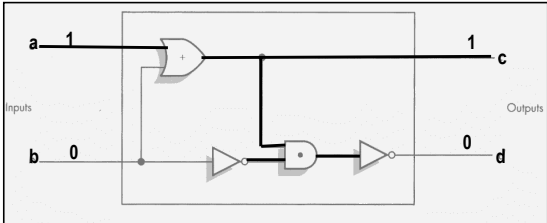**Example**

- What are the output values  $c$  and  $d$  given input values  $a=1, b=0$ ?



CMPUT101 Introduction to Computing (c) Yngvi Björnsson 7

---

---

---

---

---

---

---

---

**Circuit Diagrams and Boolean Expressions**

- The diagrams we were looking at are called circuit diagrams.
- Relationship between circuit diagrams and Boolean expr.:
  - Every Boolean expression can be represented pictorially as a circuit.
  - Every output in a circuit diagram can be written as a Boolean expression.
- Example (output values  $c$  and  $d$  from previous diagram):
  - $c = (a \text{ OR } b)$
  - $d = \text{NOT} ((a \text{ OR } b) \text{ AND } (\text{NOT } b))$

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 8

---

---

---

---

---


---

---

---

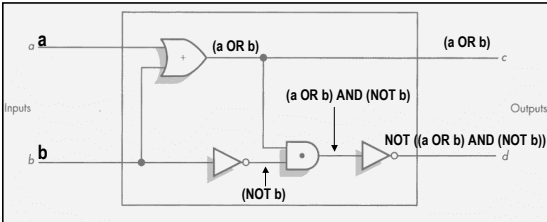**Circuits Diagram and Boolean Expressions**

- Deriving Boolean expressions for the output.



CMPUT101 Introduction to Computing (c) Yngvi Björnsson 9

---

---

---

---

---


---

---

---
 
### Circuits Diagram and Boolean Expressions

- Remember, when writing Boolean expressions for circuit diagrams, we use a different notation!



CMPUT101 Introduction to Computing (c) Yngvi Björnsson 10

---

---

---

---

---


---

---

---
 
### Example

- What Boolean expression describes the output?



CMPUT101 Introduction to Computing (c) Yngvi Björnsson 11

---

---

---

---

---

---

---

---

### Constructing Circuits

- How do we design and construct circuits?
  - We first have to know what we want the circuit to do!
  - This implies, that for all possible input combinations we must decide what the output should be.
- Once we know that, there exists methods we can use to design the layout of the circuit.
  - We will look at one such method called, sum-of-products algorithm.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 12

---

---

---

---

---

---

---

---

### Sum-of-Products Algorithm

Step 1: Truth Table Construction  
 Repeat steps 2, 3 and 4 for each output column  
     Step 2: Sub-expression construction using AND and NOT gates  
     Step 3: Sub-expression combination using OR gates  
     Step 4: Circuit Diagram Production  
 Step 5: Combine Circuit Diagrams  
 Step 6: Optimize Circuit (optional)  
 Step 7: Stop

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 13

---

---

---

---

---


---

---

---
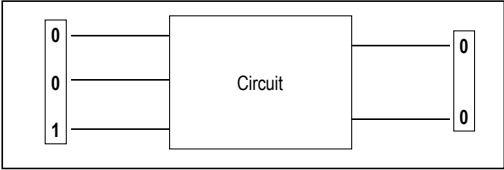
### Step 1: Truth Table Construction

- Decide what the circuit is supposed to do:
  - treat the circuit itself as a “black box”
  - only interested in input/output signals



CMPUT101 Introduction to Computing (c) Yngvi Björnsson 14

---

---

---

---

---

---

---

---

### Step 1 (cont.)

- Write the desired output for all possible input combinations:

3 inputs →  $2^3 = 8$   
possibilities

Inputs			Outputs	
a	b	c	1	2
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	0	1
1	0	0	0	0
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 15

---

---

---

---

---

---

---

---

### Step 2: Sub-expression Construction

- For each output (separately):
  - Use AND and NOT gates to construct a sub-expression for rows where the output is 1

Inputs			Outputs	
a	b	c	1	2
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	0	1
1	0	0	0	0
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0

Case 1

Case 2

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 16

---

---

---

---

---

---

---

---

---

---

---

---

### Step 2 (cont.)

- Look at the inputs, if the value is
  - 1 then use input as is in sub-expression, ( e.g.  $b$  )
  - 0 then use input value complemented ( e.g.  $\bar{a}$  )

a	b	c	1
...	...	...	...
0	1	0	1
...	...	...	...
1	1	0	1
...	...	...	...

→  $\bar{a} \cdot b \cdot \bar{c}$

→  $a \cdot b \cdot \bar{c}$

- Why do it this way?
  - Each expression will evaluate to 1 for given input combination (row), but 0 for all other inputs!

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 17

---

---

---

---

---

---

---

---

---

---

---

---

### Step 3: Sub-expression Combination

- Use OR gates to combine the sub-expressions from previous step into one expression

$$(\bar{a} \cdot b \cdot \bar{c}) + (a \cdot b \cdot \bar{c})$$

- This expression will evaluate to 1 for all input combinations that have 1 as output, but 0 for all the other input combinations (rows)!

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 18

---

---

---

---

---

---

---

---

---

---

---

---

### Step 4: Circuit Diagram Production

- Construct a circuit diagram from the expression generated in previous step:  $(\bar{a} \cdot b \cdot \bar{c}) + (a \cdot b \cdot \bar{c})$

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 19

---

---

---

---

---

---

---

---

### Repeat steps 2, 3, and 4 for each output

- We need to repeat steps 2, 3, 4 for each output.
- In our example, there is one more output:
  - Step 2: Four sub-expressions, one for each row:
 
$$\bar{a} \cdot b \cdot \bar{c} \quad \bar{a} \cdot b \cdot c \quad \bar{a} \cdot \bar{b} \cdot c \quad a \cdot b \cdot \bar{c}$$
  - Step 3: Combine sub-expressions using + (OR):
 
$$(\bar{a} \cdot b \cdot \bar{c}) + (\bar{a} \cdot b \cdot c) + (\bar{a} \cdot \bar{b} \cdot c) + (a \cdot b \cdot \bar{c})$$
  - Step 4: Draw circuit diagram

(see p. 694 in text-book)

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 20

---

---

---

---

---

---

---

---

### Combine Individual Circuits

- Combine the circuits for each individual output into an one larger circuit.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 21

---

---

---

---

---

---

---

---

### Optimize the Circuit

- A circuit build using this algorithm will generate the correct output, but it uses unnecessarily many gates
  - Why is that important?
  - Typically we need to optimize the circuit, by minimize the number of gates used.
- An optimized circuit for the example would look like:

CMPUT101 Intro 22

---

---

---

---

---

---

---

---

### Example 1: Compare-for-Equality Circuit (N-CE)

- We want to build a circuit that checks if two numbers are the same?
 

0	0	0	0	0	0	0	0	0	0	0	0	1	1	1	0
...															
0	0	0	0	0	0	0	0	0	0	0	0	1	1	1	0

  - The same number if and only if all corresponding bits are the identical.
- First step is to build a circuit that compares two bits (can then use 16 of those to compare two 16-bit numbers!)

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 23

---

---

---

---

---

---

---

---

### Ex1 --Step 1: Truth table construction

- The circuit to compare two bits has:
  - two inputs (the value of the two bits)
  - one output (0 if the bits are different, 1 if the bits are same)

- How does the truth-table look like?

Inputs		Output
a	b	
0	0	1
0	1	0
1	0	0
1	1	1

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 24

---

---

---

---

---

---

---

---



**Example 1: Step 2 Construct sub-expressions**

- Construct a Boolean expression for each row in the table where the output is one:

Inputs		Output
a	b	
0	0	1
0	1	0
1	0	0
1	1	1

=  $\bar{a}\bar{b}$

=  $a\cdot b$

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 25

---

---

---

---

---


---

---

---

 **Example 1: Step 3 and 4**

- Combine into one sub-expression using OR (+)  
 $(\bar{a}\bar{b}) + (a\cdot b)$
- Draw a circuit diagram



CMPUT101 Introduction to Computing (c) Yngvi Björnsson 26

---

---

---

---

---


---

---

---

 **Repeat for each output**

- Need to repeat step 2, 3, 4 for all outputs:
  - There is only one output, so we are done!
- So our 1-bit compare circuit ( 1-CE ) looks like:



CMPUT101 Introduction to Computing (c) Yngvi Björnsson 27

---

---

---


---

---

---

---

---

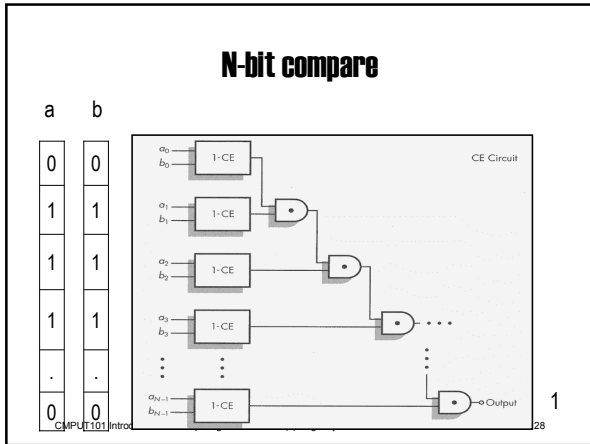


---

---

---

---

---


---

---

---

---

---

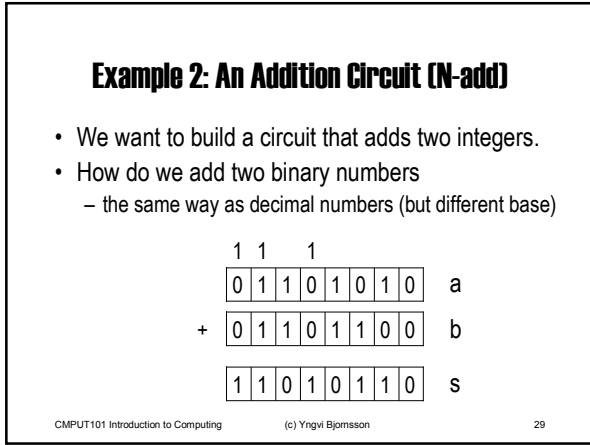


---

---

---

---

---


---

---

---

---

---

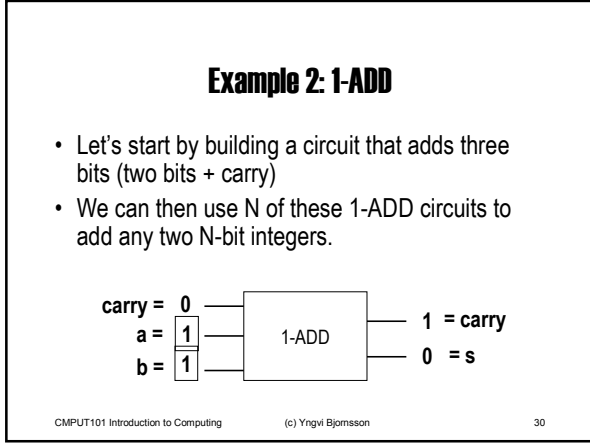


---

---

---

---

---

---

---

---

---

---

**Ex2-- Step 1: Truth table construction**

Inputs			Outputs	
a	b	c	s	c
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 31

---

---

---

---

---

---

---

---

---

---

**Example 2: Step 2-3 (output 1)**

- Construct a Boolean expression for each 1-row

Inputs			Outputs
a	b	c	s
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

- $\bar{a} \cdot \bar{b} \cdot c$
- $\bar{a} \cdot b \cdot \bar{c}$
- $a \cdot \bar{b} \cdot c$
- $a \cdot b \cdot c$

- Combine into one Boolean expression

$$s = (\bar{a} \cdot \bar{b} \cdot c) + (\bar{a} \cdot b \cdot \bar{c}) + (a \cdot \bar{b} \cdot c) + (a \cdot b \cdot c)$$

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 32

---

---

---

---

---

---


---

---

---

---

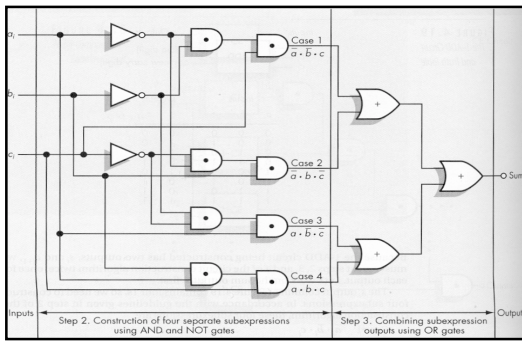**Example 2: Step 4 Circuit Diagram (output 1)**




---

---

---

---

---

---

---

---

---

---

**Example 2: Step 2-3-4 (output 2)**

- Step 2 : Construct a Boolean expression for each 1-row

a	b	c	carry
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- $\bar{a} \cdot b \cdot c$
- $a \cdot \bar{b} \cdot c$
- $a \cdot b \cdot \bar{c}$
- $a \cdot b \cdot c$

- Step 3: Combine into one Boolean expression  
 $s = (\bar{a} \cdot b \cdot c) + (a \cdot \bar{b} \cdot c) + (a \cdot b \cdot \bar{c}) + (a \cdot b \cdot c)$
- Step 4: Draw a circuit diagram (not shown)

CMPUT101 Introduction to Computing (c) Yingxi Björnsson 34

---

---

---

---

---

---


---

---

---

---

 **Example 2: Combining output 1 and 2 circuits**



35

---

---

---

---

---

---


---

---

---

---

**Example 2: N-ADD**

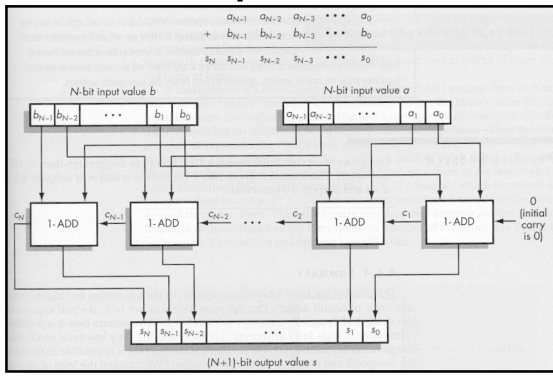


---

---

---

---

---

---

---

---

---

---

**Example 2: Optimize the circuit**

- Each 1-ADD circuit has 25 gates (47 transistors)
  - 16 AND gates ( x 2 transistors)
  - 6 OR gates ( x 2 transistors)
  - 3 NOT gates ( x 1 transistors)
- To add two 32-bits integers we need
  - 32 1-ADD circuits  $\rightarrow 32 * 25 = 800$  gates  $\rightarrow 1504$  transistors
- Optimized 32-bits addition circuit in modern computers uses: 500-600 transistors
  - We will not learn how to optimize circuits in this course

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 37

---

---

---

---

---

---

---


---

---

---

**Control Circuits**

Chapter 4.5

 


---

---

---

---

---

---

---

---

---

---

**Control Circuits**

- So far we have seen two types of circuits:
  - Logical ( is a = b ?)
  - Arithmetic ( c = a + b)
- Computers use many different logical (>, <, >=, <=, !=, ...), and arithmetic (+, -, \*, /) circuits.
- There are also different kind of circuits that are essential for computers  $\rightarrow$  control circuits
  - We will look at two different kind of control circuits, multiplexors and decoders.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 39

---

---

---

---

---

---

---

---

---

---

### Multiplexor

- A multiplexor circuit has:
  - $2^N$  input lines (numbered 0, ...,  $2^N-1$ )
  - 1 output line
  - N selector lines
- The selector lines are used to choose which of the input signals becomes the output signal:
  - Selector lines interpreted as an N-bit integer
  - The signal on the input line with the corresponding number becomes the output signal.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 40

---

---

---

---

---

---

---

---

### Multiplexor (cont.)

The diagram shows a central box labeled 'Multiplexor circuit'. On the left side, there are  $2^N$  input lines, numbered 0, 1, 2, ...,  $2^N-1$ . On the bottom side, there are N selector lines, represented by three arrows pointing up and an ellipsis. On the right side, there is one output line.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 41

---

---

---

---

---

---

---

---

### Multiplexor (cont.)

The diagram shows a box labeled 'Multiplexor'. On the left, there are four input lines numbered 0, 1, 2, and 3. Line 0 has a value of 0, line 1 has a value of 1, line 2 has a value of 0, and line 3 has a value of 1. On the bottom, there are two selector lines, both with a value of 1. On the right, there is one output line with a value of 1.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 42

---

---

---

---

---

---

---

---

### Decoder

- A decoder circuit has:
  - N input lines (numbered 0, 1, ..., N-1)
  - $2^N$  output line (numbered 0, 1, ...  $2^N-1$ )
- Works as follows:
  - The N input lines are interpreted as a N-bit integer value.
  - The output line corresponding to the integer value is set to 1, all other to 0

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 43

---

---

---

---

---

---

---

---

### Decoder (cont.)

The diagram shows a central box labeled "Decoder circuit". On the left, there are N input lines labeled 0, 1, 2, ..., N-1. On the right, there are  $2^N$  output lines labeled 0, 1, 2, ...,  $2^N-1$ .

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 44

---

---

---

---

---

---

---

---

### Decoder (cont.)

The diagram shows a 3-bit decoder circuit. On the left, three input lines are shown with values 0, 0, and 1, representing the binary number 100. Below these inputs, it says "100 = 4". The decoder has three input lines labeled 0, 1, and 2. On the right, there are eight output lines labeled 0 through 7. Output line 4 is shown with a '1', while all other output lines (0, 1, 2, 3, 5, 6, 7) are shown with a '0'.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 45

---

---

---

---

---

---

---

---

### Summary

- We looked at how computers represent data:
  - Internal vs External Representation
  - Basic storage unit is a binary digit → bit
  - Data is represented internally as binary data.
  - Use the binary number system.
- We learned why computers use binary data:
  - Main reason is reliability
  - Electronic devices work best in bi-stable environment.

CMPUT101 Introduction to Computing (c) Yngvi Bjornsson 46

---

---

---

---

---

---

---

---

### Summary (cont.)

- We looked at the basic building blocks used in computers:
  - Binary Storage Device = Transistor
- We saw how to build logic gates (AND, OR, NOT):
  - Transistors → Gates
  - Boolean logic
- We saw how to build circuits:
  - Gates → Circuits
  - Looked at logical, arithmetic, and control circuits.

CMPUT101 Introduction to Computing (c) Yngvi Bjornsson 47

---

---

---

---

---

---

---

---

### Summary (cont.)

- Now that we have seen the basic building blocks (low-level view), in the next chapter we will look at the “big picture” (high-level view).
- We will look at the basic architecture underlying design of all computers:
  - Look at higher level computer components, such as processors and memory.
  - Understand better how computers execute programs.

CMPUT101 Introduction to Computing (c) Yngvi Bjornsson 48

---

---

---

---

---

---

---

---