

Building Computer Circuits

Chapter 4.4

Purpose

- We have looked at so far how to build logic gates from transistors.
- Next we will look at how to build circuits from logic gates, for example:
 - A circuit to check if two numbers are equal.
 - A circuit to add two numbers.
- Gates will become our new building blocks:
 - Human body: cells → organs → body
 - Computers: gates → circuits → computer

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 2

Circuit

- A circuit is a collection of interconnected logic gates:
 - that transforms a set of binary inputs into a set of binary outputs, and
 - where the values of the outputs depend only on the current values of the inputs
- These kind of circuits are more accurately called combinatorial circuits.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 3

Circuit (external view)

- A circuit can have any number of inputs and outputs:
 - Number of inputs and outputs can differ.
 - The inputs and outputs are either 0 or 1.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 4

Circuit (external view cont.)

- Output depends only on current input values
 - Each set of input always generates the same output.
 - Different sets of input can generate identical output.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 5


Circuit (Internal view)

- Circuits are build from interconnected AND, OR and NOT gates, in a way such that each input combination produces the desired output.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 6

 Example

- What are the output values c and d given input values $a=1, b=0$?



CMPUT101 Introduction to Computing (c) Yngvi Björnsson 7


Circuit Diagrams and Boolean Expressions

- The diagrams we were looking at are called circuit diagrams.
- Relationship between circuit diagrams and Boolean expr.:
 - Every Boolean expression can be represented pictorially as a circuit.
 - Every output in a circuit diagram can be written as a Boolean expression.
- Example (output values c and d from previous diagram):
 - $c = (a \text{ OR } b)$
 - $d = \text{NOT}((a \text{ OR } b) \text{ AND } (\text{NOT } b))$

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 8

Circuits Diagram and Boolean Expressions

 
- Deriving Boolean expressions for the output.



CMPUT101 Introduction to Computing (c) Yngvi Björnsson 9

Circuits Diagram and Boolean Expressions

 
- Remember, when writing Boolean expressions for circuit diagrams, we use a different notation!



CMPUT101 Introduction to Computing (c) Yngvi Björnsson 10

 Example

- What Boolean expression describes the output?



CMPUT101 Introduction to Computing (c) Yngvi Björnsson 11

Constructing Circuits

- How do we design and construct circuits?
 - We first have to know what we want the circuit to do!
 - This implies, that for all possible input combinations we must decide what the output should be.
- Once we know that, there exists methods we can use to design the layout of the circuit.
 - We will look at one such method called, sum-of-products algorithm.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 12


Sum-of-Products Algorithm

Step 1: Truth Table Construction
 Repeat steps 2, 3 and 4 for each output column
 Step 2: Sub-expression construction using AND and NOT gates
 Step 3: Sub-expression combination using OR gates
 Step 4: Circuit Diagram Production
 Step 5: Combine Circuit Diagrams
 Step 6: Optimize Circuit (optional)
 Step 7: Stop

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 13

Step 1: Truth Table Construction

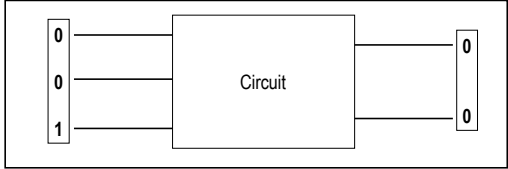- Decide what the circuit is supposed to do:
 - treat the circuit itself as a “black box”
 - only interested in input/output signals



CMPUT101 Introduction to Computing (c) Yngvi Björnsson 14

Step 1 (cont.)

- Write the desired output for all possible input combinations:

3 inputs $\rightarrow 2^3 = 8$ possibilities

Inputs			Outputs	
a	b	c	1	2
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	0	1
1	0	0	0	0
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 15

Step 2: Sub-expression Construction

- For each output (separately):
 - Use AND and NOT gates to construct a sub-expression for rows where the output is 1

Inputs			Outputs	
a	b	c	1	2
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	0	1
1	0	0	0	0
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0

← Case 1 (row 3)
← Case 2 (row 7)

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 16

Step 2 (cont.)

- Look at the inputs, if the value is
 - 1 then use input as is in sub-expression, (e.g. b)
 - 0 then use input value complemented (e.g. \bar{a})

a	b	c	1
...
0	1	0	1
...
1	1	0	1
...

$\rightarrow \bar{a} \cdot b \cdot \bar{c}$
 $\rightarrow a \cdot b \cdot \bar{c}$

- Why do it this way?
 Each expression will evaluate to 1 for given input combination (row), but 0 for all other inputs!

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 17

Step 3: Sub-expression Combination

- Use OR gates to combine the sub-expressions from previous step into one expression

$$(\bar{a} \cdot b \cdot \bar{c}) + (a \cdot b \cdot \bar{c})$$

- This expression will evaluate to 1 for all input combinations that have 1 as output, but 0 for all the other input combinations (rows)!

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 18

Step 4: Circuit Diagram Production

- Construct a circuit diagram from the expression generated in previous step: $(\bar{a} \cdot b \cdot \bar{c}) + (a \cdot b \cdot \bar{c})$

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 19

Repeat steps 2, 3, and 4 for each output

- We need to repeat steps 2, 3, 4 for each output.
- In our example, there is one more output:
 - Step 2: Four sub-expressions, one for each row: $\bar{a} \cdot \bar{b} \cdot \bar{c}$, $\bar{a} \cdot b \cdot \bar{c}$, $a \cdot b \cdot \bar{c}$, $a \cdot \bar{b} \cdot \bar{c}$
 - Step 3: Combine sub-expressions using + (OR): $(\bar{a} \cdot \bar{b} \cdot \bar{c}) + (\bar{a} \cdot b \cdot \bar{c}) + (a \cdot b \cdot \bar{c}) + (a \cdot \bar{b} \cdot \bar{c})$
 - Step 4: Draw circuit diagram (see p. 694 in text-book)

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 20

Combine Individual Circuits

- Combine the circuits for each individual output into an one larger circuit.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 21

Optimize the Circuit

- A circuit build using this algorithm will generate the correct output, but it uses unnecessarily many gates
 - Why is that important?
 - Typically we need to optimize the circuit, by minimize the number of gates used.
- An optimized circuit for the example would look like:

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 22

Example 1: Compare-for-Equality Circuit (N-CE)

- We want to build a circuit that checks if two numbers are the same?

0	0	0	0	0	0	0	0	0	0	0	0	1	1	1	0
							...								
0	0	0	0	0	0	0	0	0	0	0	0	1	1	1	0

 - The same number if and only if all corresponding bits are identical.
- First step is to build a circuit that compares two bits (can then use 16 of those to compare two 16-bit numbers!)

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 23

Ex1 -- Step 1: Truth table construction

- The circuit to compare two bits has:
 - two inputs (the value of the two bits)
 - one output (0 if the bits are different, 1 if the bits are same)

- How does the truth-table look like?

Inputs		Output
a	b	
0	0	1
0	1	0
1	0	0
1	1	1

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 24

Example 1: Step 2 Construct sub-expressions

- Construct a Boolean expression for each row in the table where the output is one:


Inputs		Output
a	b	
0	0	1
0	1	0
1	0	0
1	1	1

$\begin{matrix} \text{Row 1: } & = & \bar{a}\bar{b} \\ \text{Row 4: } & = & a\cdot b \end{matrix}$

 Example 1: Step 3 and 4


- Combine into one sub-expression using OR (+)

$$(\bar{a}\bar{b}) + (a\cdot b)$$
- Draw a circuit diagram



Repeat for each output

 
- Need to repeat step 2, 3, 4 for all outputs:
 - There is only one output, so we are done!
- So our 1-bit compare circuit (1-CE) looks like:



- But we want to compare N-bit sized numbers?

N-bit compare

a b

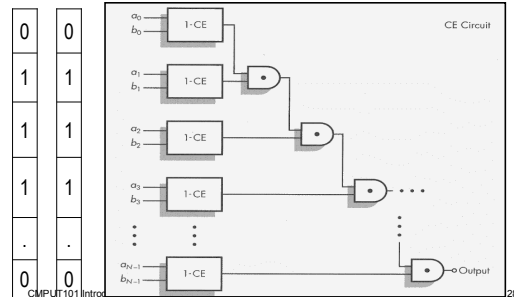

Example 2: An Addition Circuit (N-add)


- We want to build a circuit that adds two integers.
- How do we add two binary numbers
 - the same way as decimal numbers (but different base)

```

      1 1 1
    0 1 1 0 1 0 1 0  a
  + 0 1 1 0 1 1 0 0  b
  -----
    1 1 0 1 0 1 1 0  s
    
```

Example 2: 1-ADD

- Let's start by building a circuit that adds three bits (two bits + carry)
- We can then use N of these 1-ADD circuits to add any two N-bit integers.

 

Ex2--Step 1: Truth table construction

Inputs			Outputs	
a	b	c	s	c
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

CMPUT101 Introduction to Computing

(c) Yngvi Björnsson

31

Example 2: Step 2-3 (output 1)

- Construct a Boolean expression for each 1-row

a	b	c	s
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

- $\bar{a}\bar{b}c$
- $\bar{a}b\bar{c}$
- $a\bar{b}\bar{c}$
- $a\bar{b}c$

- Combine into one Boolean expression


$$s = (\bar{a}\bar{b}c) + (\bar{a}b\bar{c}) + (a\bar{b}\bar{c}) + (a\bar{b}c)$$

CMPUT101 Introduction to Computing

(c) Yngvi Björnsson

32

Example 2: Step 4 Circuit Diagram (output 1)

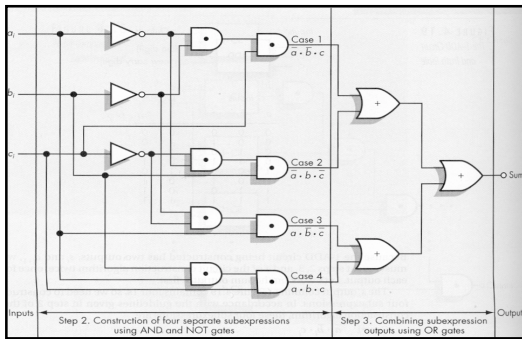

Example 2: Step 2-3-4 (output 2)

- Step 2: Construct a Boolean expression for each 1-row

a	b	c	carry
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- $\bar{a}b\bar{c}$
- $a\bar{b}c$
- $a\bar{b}\bar{c}$
- $a\bar{b}c$

- Step 3: Combine into one Boolean expression

$$s = (\bar{a}b\bar{c}) + (a\bar{b}c) + (a\bar{b}\bar{c}) + (a\bar{b}c)$$


- Step 4: Draw a circuit diagram (not shown)

CMPUT101 Introduction to Computing

(c) Yngvi Björnsson


34

 Example 2: Combining output 1 and 2 circuits



35

Example 2: N-ADD

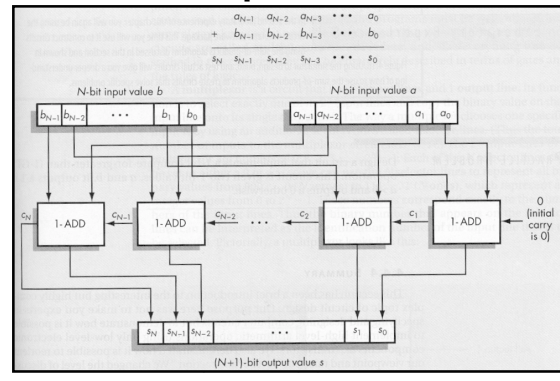


Example 2: Optimize the circuit

- Each 1-ADD circuit has 25 gates (47 transistors)
 - 16 AND gates (x 2 transistors)
 - 6 OR gates (x 2 transistors)
 - 3 NOT gates (x 1 transistors)
- To add two 32-bit integers we need
 - 32 1-ADD circuits → $32 * 25 = 800$ gates → 1504 transistors
- Optimized 32-bit addition circuit in modern computers uses: 500-600 transistors
 - We will not learn how to optimize circuits in this course

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 37

Control Circuits

Chapter 4.5

 

Control Circuits

- So far we have seen two types of circuits:
 - Logical (is $a = b$?)
 - Arithmetic ($c = a + b$)
- Computers use many different logical ($>$, $<$, $>=$, $<=$, $!=$, ...) and arithmetic ($+$, $-$, $*$, $/$) circuits.
- There are also different kind of circuits that are essential for computers → control circuits
 - We will look at two different kind of control circuits, multiplexors and decoders.


CMPUT101 Introduction to Computing (c) Yngvi Björnsson 39

Multiplexor

- A multiplexor circuit has:
 - 2^N input lines (numbered $0, \dots, 2^N-1$)
 - 1 output line
 - N selector lines
- The selector lines are used to choose which of the input signals becomes the output signal:
 - Selector lines interpreted as an N -bit integer
 - The signal on the input line with the corresponding number becomes the output signal.


CMPUT101 Introduction to Computing (c) Yngvi Björnsson 40

Multiplexor (cont.)

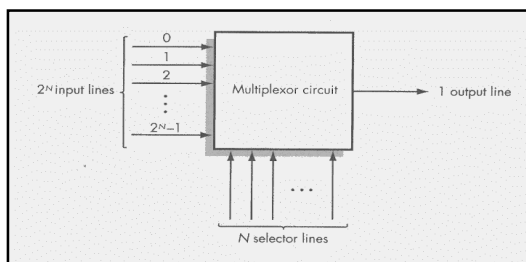

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 41

Multiplexor (cont.)

 

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 42

Decoder

- A decoder circuit has:
 - N input lines (numbered 0, 1, ..., N-1)
 - 2^N output line (numbered 0, 1, ... 2^N-1)
- Works as follows:
 - The N input lines are interpreted as a N-bit integer value.
 - The output line corresponding to the integer value is set to 1, all other to 0

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 43

Decoder (cont.)

The diagram shows a central box labeled 'Decoder circuit'. On the left, there are N input lines labeled 0, 1, 2, ..., N-1. On the right, there are 2^N output lines labeled 0, 1, 2, ..., 2^N-1 .

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 44

Decoder (cont.)

The diagram shows a 3-bit decoder circuit. On the left, there are three input lines labeled 0, 0, 1. Below them, it says '100 = 4'. On the right, there are eight output lines labeled 0 through 7. Output line 4 is the only one that is set to 1, while all other output lines are 0.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 45

Summary

- We looked at how computers represent data:
 - Internal vs External Representation
 - Basic storage unit is a binary digit → bit
 - Data is represented internally as binary data.
 - Use the binary number system.
- We learned why computers use binary data:
 - Main reason is reliability
 - Electronic devices work best in bi-stable environment.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 46

Summary (cont.)

- We looked at the basic building blocks used in computers:
 - Binary Storage Device = Transistor
- We saw how to build logic gates (AND, OR, NOT):
 - Transistors → Gates
 - Boolean logic
- We saw how to build circuits:
 - Gates → Circuits
 - Looked at logical, arithmetic, and control circuits.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 47

Summary (cont.)

- Now that we have seen the basic building blocks (low-level view), in the next chapter we will look at the “big picture” (high-level view).
- We will look at the basic architecture underlying design of all computers:
 - Look at higher level computer components, such as processors and memory.
 - Understand better how computers execute programs.

CMPUT101 Introduction to Computing (c) Yngvi Björnsson 48